

RH850/F1L, F1M, F1H

A/D Converter Equivalent Input Circuit

R01AN3147EJ0100
Rev.1.00
Feb 17, 2016

Introduction

This document describes the equivalent input circuit of the A/D Converter.

It should be used in conjunction with the corresponding RH850/F1x series user manuals and datasheets.

Target Device

RH850/F1L Group

- RH850/F1L (176pin)
- RH850/F1L (144pin)
- RH850/F1L (100pin), including RH850/F1L-Gateway (100pin)
- RH850/F1L (80pin)
- RH850/F1L (64pin)
- RH850/F1L (48pin)

RH850/F1M Group

- RH850/F1M (233pin)
- RH850/F1M (176pin)
- RH850/F1M (144pin)

RH850/F1H Group

- RH850/F1H (272pin)
- RH850/F1H (233pin), including RH850/F1H-Gateway (233pin)
- RH850/F1H (176pin), including RH850/F1H-Gateway (176pin)

1. Reference Documents

This chapter contains information about the device reference documentation.

1.1 User's Manual

The user manual provides information about the functional behaviour of the device.

RH850/F1L User's Manual :	R01UH0390EJxxxx
RH850/F1M User's Manual :	R01UH0518EJxxxx
RH850/F1H User's Manual :	R01UH0445EJxxxx

1.2 Data Sheet

The data sheet provides information about the electrical behaviour of the device.

RH850/F1L (176pin) Data Sheet :	R01DS0170EJxxxx
RH850/F1L (144pin) Data Sheet :	R01DS0210EJxxxx
RH850/F1L (100pin) Data Sheet :	R01DS0211EJxxxx
RH850/F1L (80pin) Data Sheet :	R01DS0212EJxxxx
RH850/F1L (64pin) Data Sheet :	R01DS0213EJxxxx
RH850/F1L (48pin) Data Sheet :	R01DS0214EJxxxx
RH850/F1M Data Sheet :	R01DS0250EJxxxx
RH850/F1H Data Sheet :	R01DS0234EJxxxx

2. A/D Converter Equivalent Input Circuit

This chapter contains the reference values of the A/D Converter equivalent input circuit.

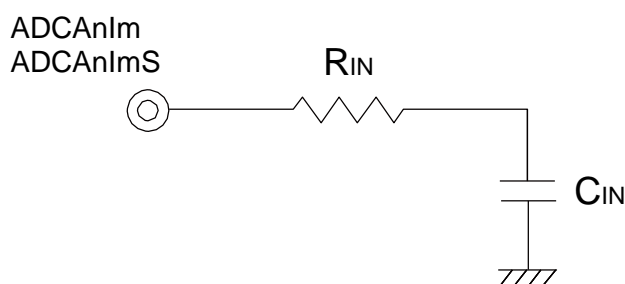


Figure 2-1 ADCAnIm, ADCAnImS Equivalent Input Circuit

2.1 RH850/F1L 176pin, 144pin

Terminals	Condition	R_{IN} (k Ω)	C_{IN} (pF)
ADCA0I0-15	When T&H is used	14.1	2.2
	When T&H is not used	5.0	2.1
ADCA0I0S to 3S, 5S to 16S	-	7.2	8.4
ADCA0I4S, 17S to 19S	-	10.0	8.4
ADCA1I0 to15	-	4.3	3.1
ADCA1I0S to 7S	-	5.6	6.2

Caution

This specification is not tested during outgoing inspection. Therefore R_{IN} and C_{IN} are reference values only and not guaranteed. In addition these values are specified as maximum values.

2.2 RH850/F1L 100pin, 80pin, 64pin, 48pin

Terminals	Condition	R_{IN} (k Ω)	C_{IN} (pF)
ADCA0I0-15	When T&H is used	14.1	2.2
	When T&H is not used	4.6	2.1
ADCA0I0S to 3S, 5S to 16S	-	6.8	8.8
ADCA0I4S, 17S to 19S	-	9.4	8.8

Caution

This specification is not tested during outgoing inspection. Therefore R_{IN} and C_{IN} are reference values only and not guaranteed. In addition these values are specified as maximum values.

2.3 RH850/F1M

Terminals	Condition	R_{IN} (k Ω)	C_{IN} (pF)
ADCA0I0-15	When T&H is used	13.9	2.6
	When T&H is not used	4.5	2.2
ADCA0I0S to 3S, 5S to 11S, 14S to 16S	-	6.1	9.4
ADCA0I4S, 17S to 19S	-	8.8	9.4
ADCA1I0 to15	-	4.2	2.2
ADCA1I0S to 10S	-	8.3	8.5
ADCA1I11S to 19S	-	6.0	8.6

Caution

This specification is not tested during outgoing inspection. Therefore R_{IN} and C_{IN} are reference values only and not guaranteed. In addition these values are specified as maximum values.

2.4 RH850/F1H

Terminals	Condition	R_{IN} (k Ω)	C_{IN} (pF)
ADCA0I0-15	When T&H is used	13.9	2.6
	When T&H is not used	5.1	2.2
ADCA0I0S to 3S, 5S to 11S, 14S to 16S	-	6.1	9.4
ADCA0I4S, 17S to 19S	-	8.8	9.4
ADCA1I0 to15	-	4.5	2.2
ADCA1I0S to 10S	-	8.3	8.5
ADCA1I11S to 19S	-	6.0	8.6

Caution

This specification is not tested during outgoing inspection. Therefore R_{IN} and C_{IN} are reference values only and not guaranteed. In addition these values are specified as maximum values.

Revision History

Rev	Date	Descriptions	
		Page	Summary
1.00	Feb 17, 2016	-	Initial release

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation of these circuits, software, and information in the design of your equipment. Renesas Electronics assumes no responsibility for any losses incurred by you or third parties arising from the use of these circuits, software, or information.
 2. Renesas Electronics has used reasonable care in preparing the information included in this document, but Renesas Electronics does not warrant that such information is error free. Renesas Electronics assumes no liability whatsoever for any damages incurred by you resulting from errors in or omissions from the information included herein.
 3. Renesas Electronics does not assume any liability for infringement of patents, copyrights, or other intellectual property rights of third parties by or arising from the use of Renesas Electronics products or technical information described in this document. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
 4. You should not alter, modify, copy, or otherwise misappropriate any Renesas Electronics product, whether in whole or in part. Renesas Electronics assumes no responsibility for any losses incurred by you or third parties arising from such alteration, modification, copy or otherwise misappropriation of Renesas Electronics product.
 5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The recommended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.
 "Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; and industrial robots etc.
 "High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control systems; anti-disaster systems; anti-crime systems; and safety equipment etc.
 Renesas Electronics products are neither intended nor authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems, surgical implantations etc.), or may cause serious property damages (nuclear reactor control systems, military equipment etc.). You must check the quality grade of each Renesas Electronics product before using it in a particular application. You may not use any Renesas Electronics product for any application for which it is not intended. Renesas Electronics shall not be in any way liable for any damages or losses incurred by you or third parties arising from the use of any Renesas Electronics product for which the product is not intended by Renesas Electronics.
 6. You should use the Renesas Electronics products described in this document within the range specified by Renesas Electronics, especially with respect to the maximum rating, operating supply voltage range, movement power voltage range, heat radiation characteristics, installation and other product characteristics. Renesas Electronics shall have no liability for malfunctions or damages arising out of the use of Renesas Electronics products beyond such specified ranges.
 7. Although Renesas Electronics endeavors to improve the quality and reliability of its products, semiconductor products have specific characteristics such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Further, Renesas Electronics products are not subject to radiation resistance design. Please be sure to implement safety measures to guard them against the possibility of physical injury, and injury or damage caused by fire in the event of the failure of a Renesas Electronics product, such as safety design for hardware and software including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult, please evaluate the safety of the final products or systems manufactured by you.
 8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. Please use Renesas Electronics products in compliance with all applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive. Renesas Electronics assumes no liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
 9. Renesas Electronics products and technology may not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You should not use Renesas Electronics products or technology described in this document for any purpose relating to military applications or use by the military, including but not limited to the development of weapons of mass destruction. When exporting the Renesas Electronics products or technology described in this document, you should comply with the applicable export control laws and regulations and follow the procedures required by such laws and regulations.
 10. It is the responsibility of the buyer or distributor of Renesas Electronics products, who distributes, disposes of, or otherwise places the product with a third party, to notify such third party in advance of the contents and conditions set forth in this document. Renesas Electronics assumes no responsibility for any losses incurred by you or third parties as a result of unauthorized use of Renesas Electronics products.
 11. This document may not be reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
 12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products, or if you have any other inquiries.
- (Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its majority-owned subsidiaries.
 (Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.



SALES OFFICES

Renesas Electronics Corporation

<http://www.renesas.com>

Refer to "http://www.renesas.com/" for the latest and detailed information.

California Eastern Laboratories, Inc.4590 Patrick Henry Drive, Santa Clara, California 95054-1817, U.S.A.
Tel: +1-408-919-2500, Fax: +1-408-988-0279**Renesas Electronics Europe Limited**Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K.
Tel: +44-1628-585-100, Fax: +44-1628-585-900**Renesas Electronics Europe GmbH**Arcadiastrasse 10, 40472 Düsseldorf, Germany
Tel: +49-211-6503-0, Fax: +49-211-6503-1327**Renesas Electronics (China) Co., Ltd.**Room 1709, Quantum Plaza, No.27 ZhiChunLu Haidian District, Beijing 100191, P.R.China
Tel: +86-10-8235-1155, Fax: +86-10-8235-7679**Renesas Electronics (Shanghai) Co., Ltd.**Unit 301, Tower A, Central Towers, 555 Langao Road, Putuo District, Shanghai, P. R. China 200333
Tel: +86-21-2226-0888, Fax: +86-21-2226-0999**Renesas Electronics Hong Kong Limited**Unit 1601-1611, 16/F., Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong
Tel: +852-2265-6688, Fax: +852 2886-9022**Renesas Electronics Taiwan Co., Ltd.**13F, No. 363, Fu Shing North Road, Taipei 10543, Taiwan
Tel: +886-2-8175-9600, Fax: +886 2-8175-9670**Renesas Electronics Singapore Pte. Ltd.**80 Bendemeer Road, Unit #06-02 Hyflux Innovation Centre, Singapore 339949
Tel: +65-6213-0200, Fax: +65-6213-0300**Renesas Electronics Malaysia Sdn.Bhd.**Unit 1207, Block B, Menara Amcorp, Amcorp Trade Centre, No. 18, Jln Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia
Tel: +60-3-7955-9390, Fax: +60-3-7955-9510**Renesas Electronics India Pvt. Ltd.**No.777C, 100 Feet Road, HALII Stage, Indiranagar, Bangalore, India
Tel: +91-80-67208700, Fax: +91-80-67208777**Renesas Electronics Korea Co., Ltd.**12F., 234 Teheran-ro, Gangnam-Gu, Seoul, 135-080, Korea
Tel: +82-2-558-3737, Fax: +82-2-558-5141